

CSE306 - Computer Architecture Sessional

Assignment 3

8-bit MIPS Design and Simulation

Submitted by:

1805038 – Iftekhar E Mahbub Zeeon

1805049 - Somonidro Roy

1805050 - Salman Khondoker

1805053 - HAZ. Sameen Shahgir

1805055 - Shamit Fatin

17 August 2022

1. Introduction

Microprocessor without Interlocked Pipe-lined Stages (MIPS) is a Reduced Instruction Set Computer (RISC) Instruction Set Architecture (ISA). In this assignment, we implement a Processor both in software and hardware that operates on a simplified ISA based on MIPS with the 16-bit instructions of the following formats.

• R-type	<table><tr><td>Opcode</td><td>Src Reg 1</td><td>Src Reg 2</td><td>Dst Reg</td></tr><tr><td>4-bits</td><td>4-bits</td><td>4-bits</td><td>4-bits</td></tr></table>	Opcode	Src Reg 1	Src Reg 2	Dst Reg	4-bits	4-bits	4-bits	4-bits
Opcode	Src Reg 1	Src Reg 2	Dst Reg						
4-bits	4-bits	4-bits	4-bits						
• S-type	<table><tr><td>Opcode</td><td>Src Reg 1</td><td>Dst Reg</td><td>Shamt</td></tr><tr><td>4-bits</td><td>4-bits</td><td>4-bits</td><td>4-bits</td></tr></table>	Opcode	Src Reg 1	Dst Reg	Shamt	4-bits	4-bits	4-bits	4-bits
Opcode	Src Reg 1	Dst Reg	Shamt						
4-bits	4-bits	4-bits	4-bits						
• I-type	<table><tr><td>Opcode</td><td>Src Reg 1</td><td>Src Reg 2/Dst Reg</td><td>Addr./Immdt.</td></tr><tr><td>4-bits</td><td>4-bits</td><td>4-bits</td><td>4-bits</td></tr></table>	Opcode	Src Reg 1	Src Reg 2/Dst Reg	Addr./Immdt.	4-bits	4-bits	4-bits	4-bits
Opcode	Src Reg 1	Src Reg 2/Dst Reg	Addr./Immdt.						
4-bits	4-bits	4-bits	4-bits						
• J-type	<table><tr><td>Opcode</td><td>Target Jump Address</td><td>0</td></tr><tr><td>4-bits</td><td>8-bits</td><td>4-bits</td></tr></table>	Opcode	Target Jump Address	0	4-bits	8-bits	4-bits		
Opcode	Target Jump Address	0							
4-bits	8-bits	4-bits							

Some of the key specifications of this project are:

- 8-bit Data bus
- 16-bit Address bus
- 4-bit ALU
- Support for 16 operations in hardware
- Can simulate stack operations through lw and sw.

2. Instruction Set:


Section A2 Group 3 Instruction Set Assignment: BDEFPIOLHCNJKAGM

Control Word


11	10	9	8	6	7	5	4	3	2	1	0
Reg Dst	Jump	BEQ	BNEQ	MemRead	MemWrite	Mem- toReg	ALU Op(2)	ALU Op(1)	ALU Op(0)	ALU- Src	Reg- Write

ID	Name	Type	Opcode	Control Word (Bin)	Control Word (Hex)
B	addi	I	0000	0000 0000 0011	003
D	subi	I	0001	0000 0000 0111	007
E	and	R	0010	1000 0000 1001	809
F	andi	I	0011	0000 0000 1011	00b
P	j	J	0100	0100 0000 0000	400
I	sll	R	0101	0000 0001 0111	017
O	bneq	I	0110	0001 0000 0100	104
L	lw	S	0111	0000 1100 0011	0c3
H	ori	I	1000	0000 0000 1111	00f
C	sub	R	1001	1000 0000 0101	805
N	beq	I	1010	0010 0000 0100	204
J	srl	R	1011	0000 0001 1011	01b
K	nor	R	1100	1000 0001 0001	811
A	add	R	1101	1000 0000 0001	801
G	or	R	1110	1000 0000 1101	80d
M	sw	S	1111	0000 0010 0010	022


3. Circuit Diagram

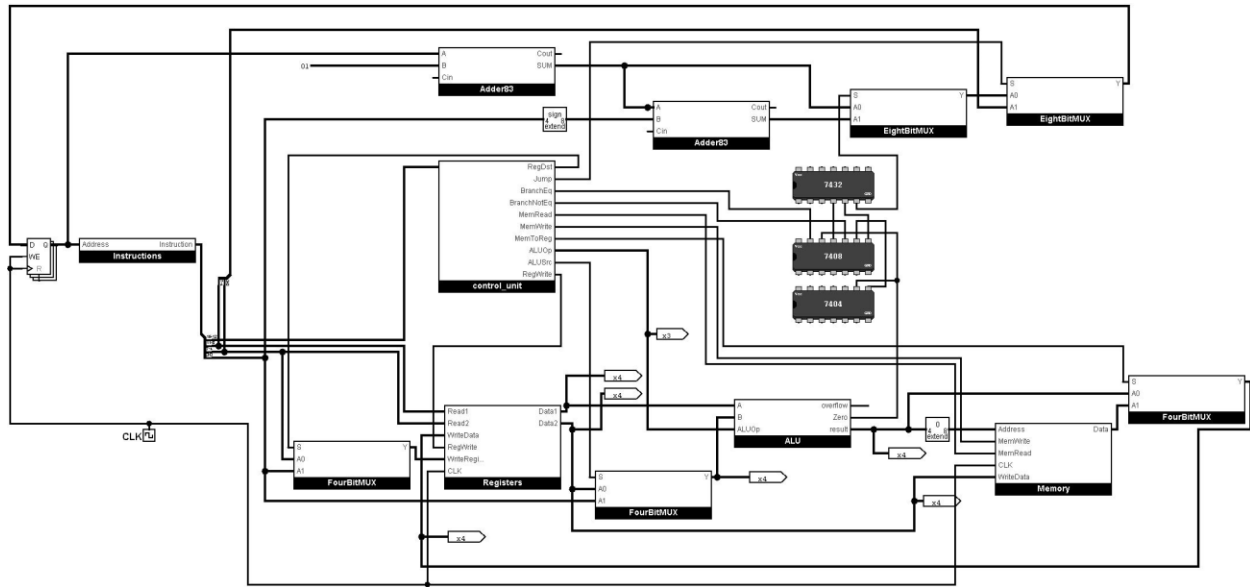


ALU:

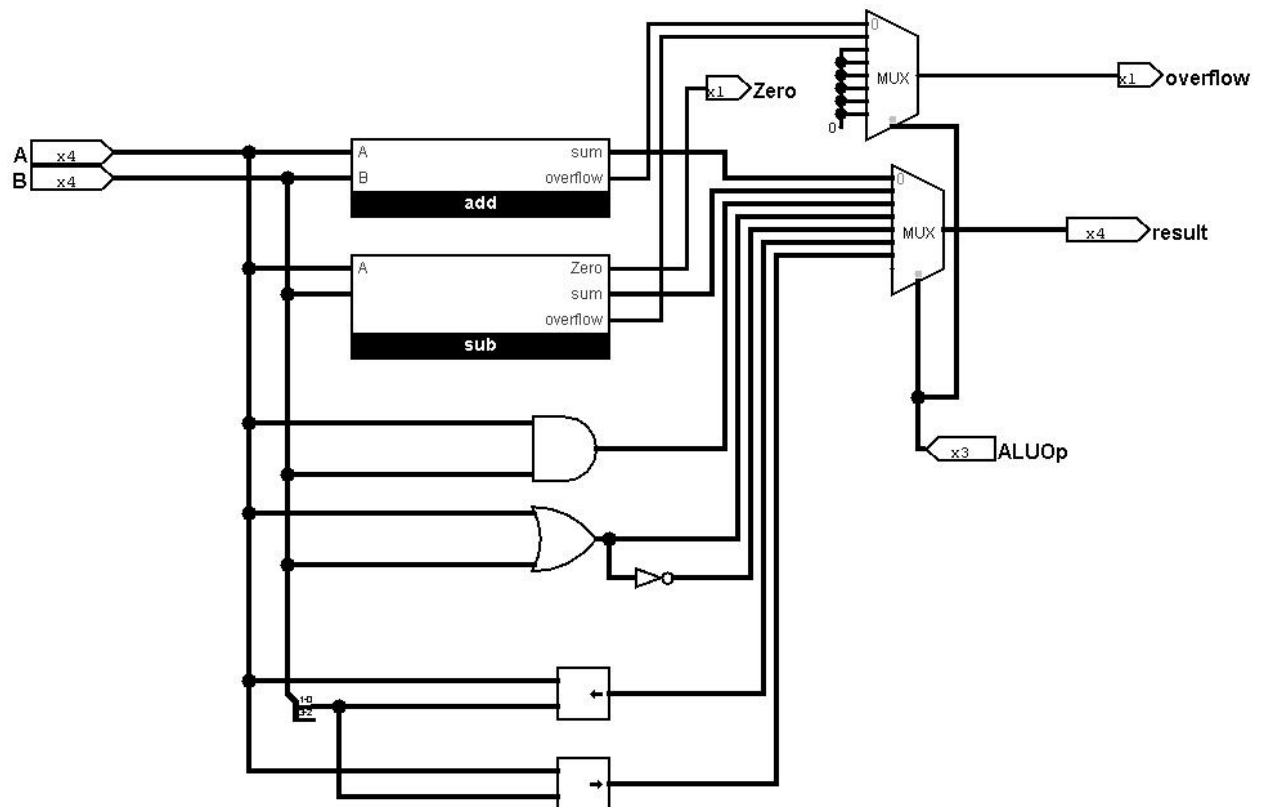


Register File:

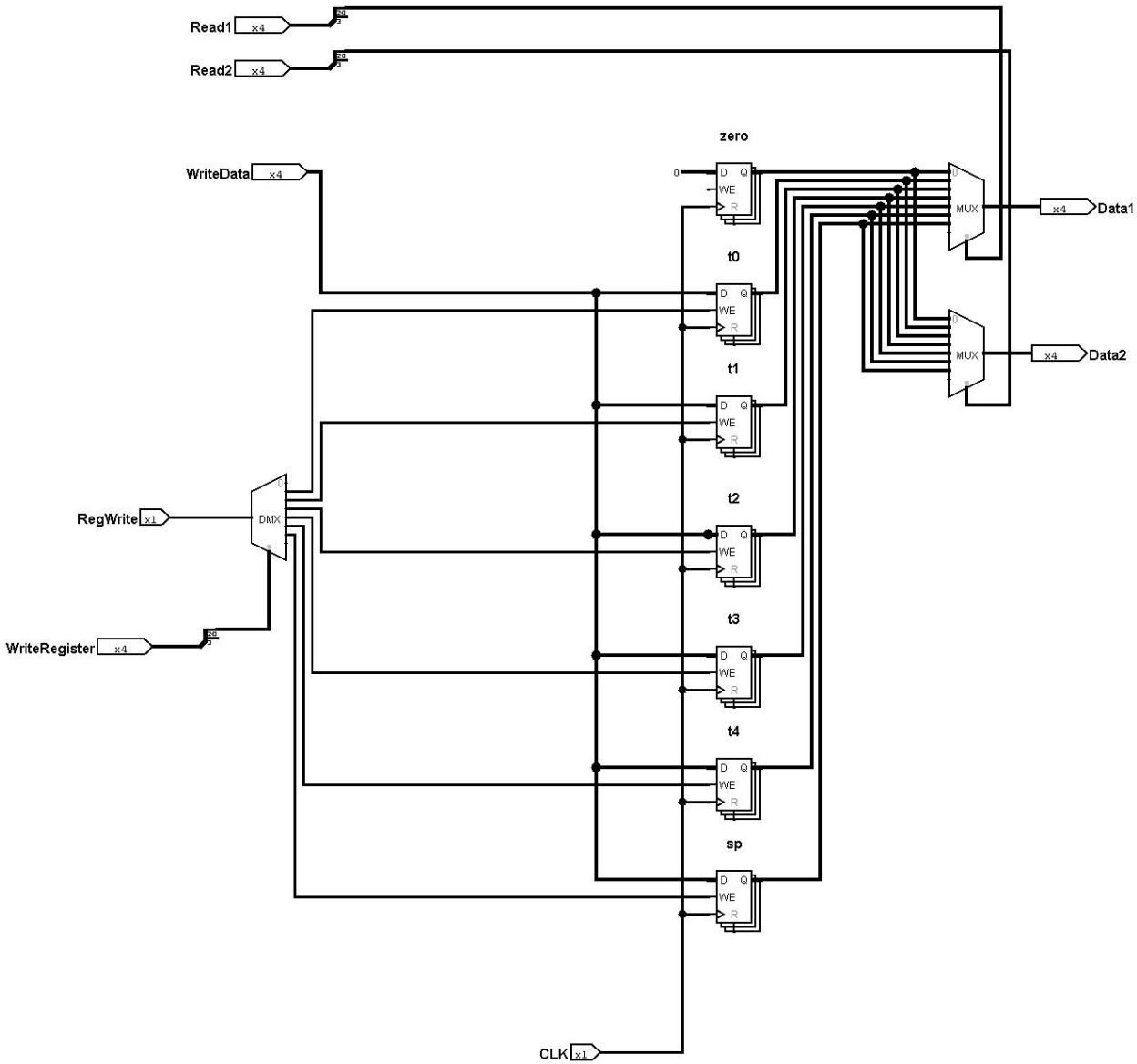

Control Unit:

 

Memory File:

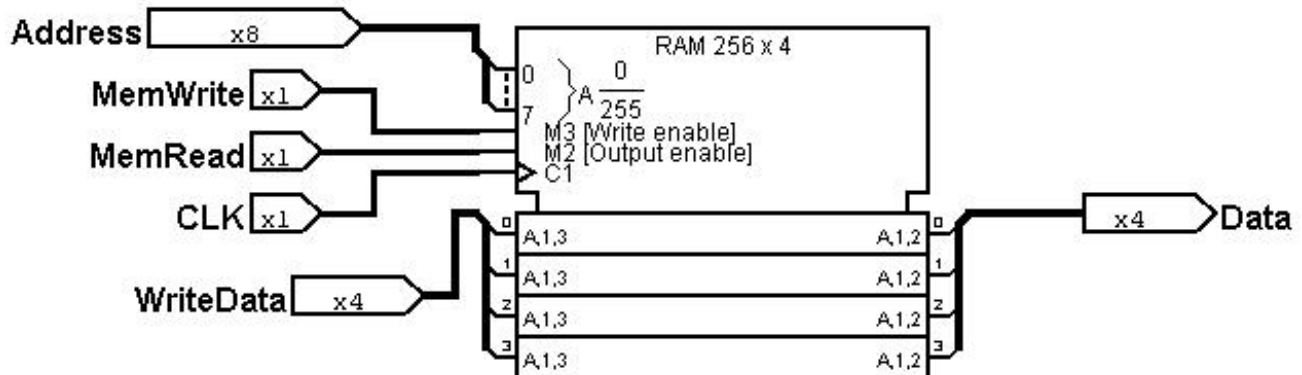

4. Program Creation and Execution

- Write the assembly code in a [file_name].txt file
- Compile mips2hex.cpp: **g++ mips2hex.cpp**
- Run the command: **./a.exe [file_name]**
- A hex.txt file should automatically be created in the current directory.
- Flash the hex code in the instructions.txt into the Instruction EEPROM
- The processor is now ready to execute.
- Step through the instructions one at a time using the Clock Pulse button.
- Instruction, Control, ALU, Register and Memory contents are displayed with LEDS

5. Special Features

The microprocessor supports stack operations using a dedicated stack pointer \$sp. Since the 4-bit ALU can address 16 memory addresses, we start inserting into stack from address 1111 (15) and continue backwards. Each stack operation is replaced by two instructions by the assembler. For example:

sw \$t1, 0(\$sp)	=	sw \$t1, 0(\$sp)	subi \$sp, \$sp, 1
lw \$t1, 4(\$sp)	=	lw \$t1, 1(\$sp)	addi \$sp, \$sp, 1

6. IC User with Count

IC	Type	Count
ATMEGA32	ROM/RAM/ALU emulation	4
74157	Quad 2x1 MUX	7
7483	4 Bit Adder	5
7432	Quad OR Gate	1
7404	Quad NOT Gate	4
7408	Quad AND Gate	1
74138	3Bit Decoder	1
74151	3to8 MUX	8
7474	D Flip Flop	12

7. Discussion:

- We noticed that to achieve 1 CPI for all instructions, the memory needs to be read at the rising edge of the clock pulse and the registers need to be written to at the falling edge.
- As per problem specification, the address bus is 8 bits long. A total of 256 instructions can be loaded at once and the Memory File has $256 \times 4 = 1024$ bits total capacity. However, since the ALU output is 4 bits, which is zero extended to 8 bits, only the first 16 addresses can be accessed.
- For *serial left shift* [sll] and *serial right shift* [srl] operations, if the shift amount exceeds 3, we have taken to be *modulo 4*. For example, **sll \$t0, \$t1, 7** is executed as **sll \$t0, \$t1, 3** since $7 \% 4 = 3$. This was done because in shifter IC chips, the shift amount cannot exceed the operand bit size.
- For branching operations [beq] and [bneq], the offset is sign extended. This allows branching 8 instructions backwards and 7 instructions forward.
- Due to the market scarcity of 4-bit ALU **IC 74181** chip, it had to be simulated using an **ATMEGA32**. The **ATMEGA32** also performs the shift operations which are not natively supported in **IC 74181**.
- Due to the market scarcity of parallel **EEPROM**, the Control Unit, Instruction File and Memory File had to be simulated using **ATMEGA32**. The clock cycle of the microcontroller is 1MHz and hence fast enough that operations appear instantaneous as in the combinatorial circuits it replaces.
- The two additional Adders used for PC increment and branching were implemented using only **IC 7483**.
- The overall design philosophy was to create the processor in such a way that the **ATMEGA32** could be easily replaced with their corresponding IC chips, hence staying true to the intention of this assignment: *building a processor from the ground up*.